

PHYSICS 231 - Solution Key to the Final Exam

1a. If you connect N bulbs each of resistance R in series to a battery of emf \mathcal{E} , the current is

$$I = \frac{\mathcal{E}}{NR}$$

The power in each bulb is

$$P = I^2 R = \frac{\mathcal{E}^2}{N^2 R}$$

As N increases, P decreases, so each bulb gets dimmer.

1b. The resistance is

$$R = \frac{\rho L}{A}$$

The power is $P = \mathcal{E}^2/R$. With a larger \mathcal{E} , we can use larger R . Since $R \propto 1/A$, larger R means smaller A , so thinner wire.

1c. No. In fact, the particle can move along the field lines. This requires no force, because $\vec{F} = q\vec{v} \times \vec{B} = \vec{0}$, if \vec{v} is along \vec{B} .

1d. We have

$$\tan \phi = \frac{X_L - X_C}{R}$$

At resonance, $X_L = X_C$. If we are far from resonance, $X_L - X_C$ is not small. If R is small, then $\tan \phi \rightarrow \infty$, so

$$\phi \approx 90^\circ$$

The power factor is $\cos \phi \approx \cos 90^\circ = 0$. Very little power is lost.

2a. The electric field due to q_1 is

$$\vec{E}_1 = \frac{kq_1}{d_1^2} \hat{x}$$

The electric field due to q_2 is

$$\vec{E}_2 = \frac{kq_2}{d_2^2} (-\hat{x})$$

The total electric field is


$$\vec{E} = \vec{E}_1 + \vec{E}_2 = 8.988 \times 10^9 \left(\frac{2.5 \times 10^{-6}}{3.5^2} + \frac{1.5 \times 10^{-6}}{0.9^2} \right) \hat{x} = (1.8 \times 10^4 \text{ N/C}) \hat{x}$$

2b. The force is

$$\vec{F} = (-e)\vec{E} = -1.6 \times 10^{-19} \times 1.8 \times 10^4 \hat{x} = -(3 \times 10^{-15} \text{ N}) \hat{x}$$

2c. The work done is equal to the potential energy of the electron,
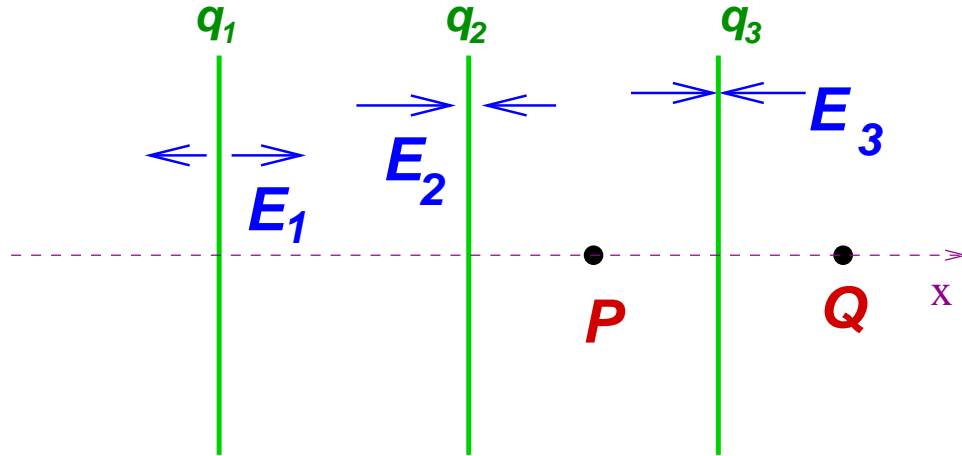
$$\begin{aligned}
 U &= k \frac{(-e)q_1}{d_1} + k \frac{(-e)q_2}{d_2} \\
 &= 8.988 \times 10^9 \times (-1.6 \times 10^{-19}) \left(\frac{2.5 \times 10^{-6}}{3.5} + \frac{-1.5 \times 10^{-6}}{0.9} \right) \\
 &= 1.37 \times 10^{-15} \text{ J}
 \end{aligned}$$



3a.

$$\sigma_1 = \frac{q_1}{A} = 1.7 \mu\text{C}/\text{m}^2, \quad \sigma_2 = \frac{q_2}{A} = -1.1 \mu\text{C}/\text{m}^2, \quad \sigma_3 = \frac{q_3}{A} = -0.6 \mu\text{C}/\text{m}^2$$

3b. Magnitude of electric field due to each sheet:

$$E_1 = \frac{|\sigma_1|}{2\epsilon_0} = 9.7 \times 10^4 \text{ N/C}, \quad E_2 = \frac{|\sigma_2|}{2\epsilon_0} = 6.5 \times 10^4 \text{ N/C}, \quad E_3 = \frac{|\sigma_3|}{2\epsilon_0} = 3.2 \times 10^4 \text{ N/C}$$

Direction as shown.

At P,


$$\vec{E} = (E_1 - E_2 + E_3) \hat{x} = (6.4 \times 10^4 \text{ N/C}) \hat{x}$$

At Q,

$$\vec{E} = (E_1 - E_2 - E_3) \hat{x} = \vec{0}$$

3c.
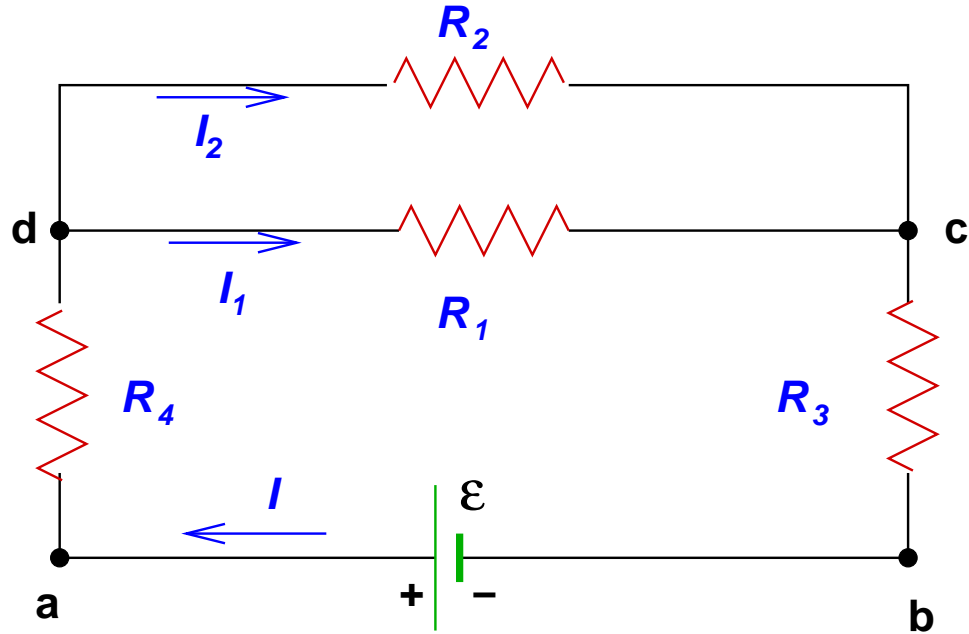
$$\vec{F} = q_2(E_1\vec{x} + E_3\vec{x}) = (-0.5 \text{ N}) \hat{x}$$



4a. R_1 and R_2 are in parallel, so the resistance between c and d is

$$R_{cd} = \frac{1}{1/R_1 + 1/R_2} = \frac{1}{1/4 + 1/2} = 1.33 \Omega$$

The total resistance is

$$R = R_4 + R_{cd} + R_3 = 4 + 1.33 + 2 = 7.33 \Omega$$

The current I is

$$I = \frac{\mathcal{E}}{R} = \frac{24}{7.33} = 3.27 \text{ A}$$

At the junction d it splits,

$$I = I_1 + I_2$$

We have

$$V_{dc} = I_1 R_1 = I_2 R_2 = I R_{cd}$$

so


$$I_1 = I \frac{R_{cd}}{R_1} = 3.27 \times \frac{1.33}{4} = 1.09 \text{ A} , \quad I_2 = I - I_1 = 2.18 \text{ A}$$

4b.

$$V_{cd} = -I_1 R_1 = -1.09 \times 4 = -4.36 \text{ V}$$

4c.
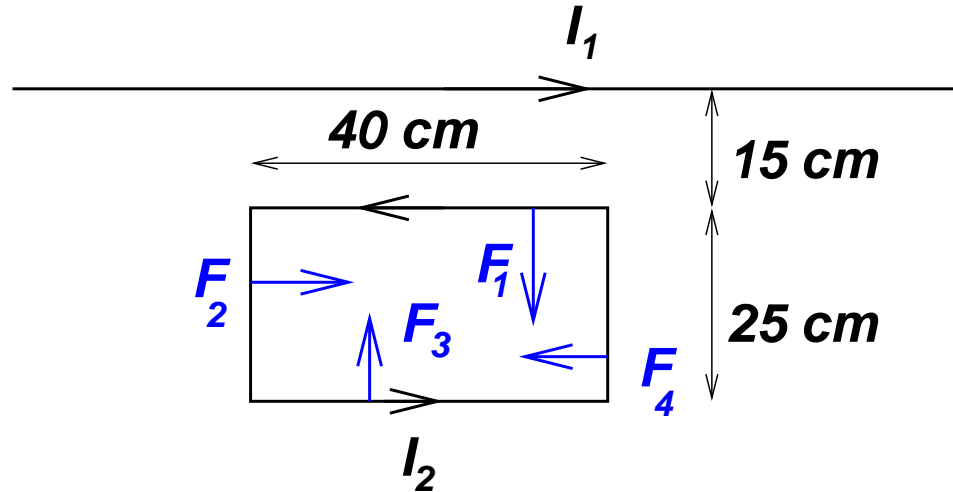
$$P = I^2 R = (3.27)^2 \times 7.33 = 78 \text{ W}$$



5. Magnetic field due to straight wire:

$$B(r) = \frac{\mu_0 I_1}{2\pi r}$$

Magnitudes of forces:

$$F_1 = I_2 L B(r_1) \quad , \quad F_2 = I_2 L B(r_2)$$

where $L = 40 \text{ cm}$ and $r_1 = 15 \text{ cm}$, $r_2 = 15 + 25 = 40 \text{ cm}$.

The other two forces, F_2 and F_4 are harder to calculate but they cancel each other. Since $F_1 > F_2$, the net force has magnitude

$$F = F_1 - F_2 = \frac{\mu_0 L I_1 I_2}{2\pi r_1} - \frac{\mu_0 L I_1 I_2}{2\pi r_2} = \frac{4\pi \times 10^{-7} \times 0.40 \times 3 \times 1.8}{2\pi} \left(\frac{1}{0.15} - \frac{1}{0.40} \right) = 1.8 \times 10^{-6} \text{ N}$$

and direction same as \vec{F}_1 .

6a.

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad , \quad \tau = \frac{L}{R}$$

At $t = 0 \text{ s}$, $I = 0 \text{ A}$.

At $t = 0.05 \text{ s}$,

$$I = \frac{40}{200} (1 - e^{-200 \times 0.05/5}) = 0.17 \text{ A}$$

At $t \rightarrow \infty$,

$$I = \frac{\mathcal{E}}{R} = \frac{40}{200} = 0.2 \text{ A}$$

6b. $U = \frac{1}{2} L I^2$

At $t = 0 \text{ s}$, $U = 0 \text{ J}$.

At $t = 0.05 \text{ s}$,

$$U = \frac{1}{2} \times 5 \times (0.17)^2 = 0.07 \text{ J}$$

At $t \rightarrow \infty$,

$$U = \frac{1}{2} \times 5 \times (0.2)^2 = 0.1 \text{ J}$$